

# 大同大學 100 學年度轉學入學考試試題

考試科目：電子學

所別：電機工程學系

第 1/1 頁

註：本次考試 不可以參考自己的書籍及筆記；不可以使用字典；可以使用計算器。

1. Refer to Fig. P1, diode with cut-in voltage  $V_{D0}=0.7$  V, diode reresistance  $r_D=0$ ,  $V_{B1}=V_{B2}=4.3$  V,

(a). Draw VTC (i.e.  $v_o$  vs  $v_I$ ) plot, indicate the breakpoint voltage clearly. (10%)

(b).  $v_I(t)=10\sin\omega t$  Volt, draw the output waveform,  $v_o$  vs  $\omega t$  for  $0 \leq \omega t \leq 4\pi$ . (10%)

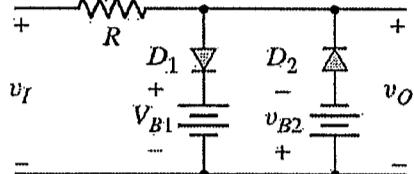


Fig. P1

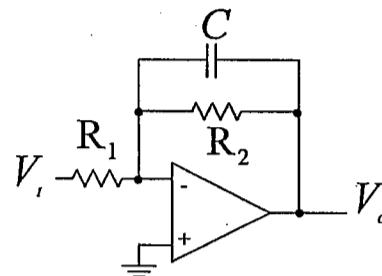


Fig. P2

2. (a). Refer to Fig. P2, for ideal OP amp, derive the transfer function  $A(s)=V_O/V_I$ . (8%)

(b). Design the circuit to obtain the input resistance of  $2\text{K}\Omega$ , a dc gain of  $40\text{dB}$ , and a 3-dB frequency of  $4\text{KHz}$  (i.e. calculate  $R_1, R_2$  and  $C$ ). (9%) Calculate the unity gain frequency  $f_u$ ? (3%)

3. Refer to Fig. P3, BJT  $\beta=100$ , neglect BJT Early effect,  $I_R=1\text{mA}$ ,  $R_s=5\text{K}\Omega$ ,  $R_B=100\text{k}\Omega$ ,  $R_C=8\text{k}\Omega$ ,  $R_L=5\text{k}\Omega$ .

(a). Draw the small-signal equivalent circuit. (3%).

(b). Calculate voltage gain  $A_v=\frac{v_o}{v_i}$  (12%) and input resistance  $R_{in}$ . (5%)

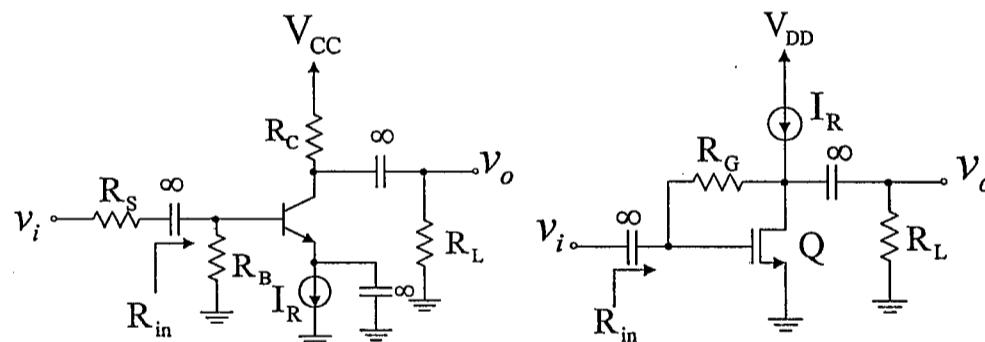


Fig. P3

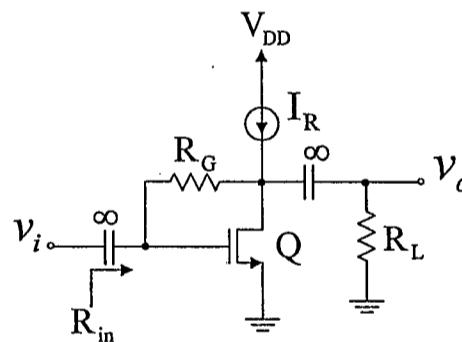


Fig. P4

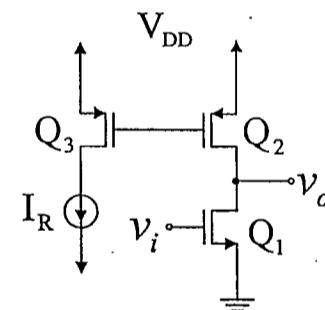


Fig. P5

4. Refer to Fig. P4, nMOS,  $I_R=500\mu\text{A}$ ,  $V_{tn}=0.9$  V,  $R_G=10\text{M}\Omega$ ,  $R_L=10\text{k}\Omega$ ,  $V_A=50\text{V}(\frac{1}{\lambda})$ ,

$$\mu_n C_{ox} W/L = 2\text{mA/V}^2$$

(a). Draw the small-signal equivalent circuit. (3%)

(b). Calculate the midband voltage gain  $A_v=\frac{v_o}{v_i}$  (12%) and input resistance  $R_{in}$ . (5%)

5. Refer to Fig. P5,  $I_R=100\mu\text{A}$ ,  $\mu_n C_{ox}=200\mu\text{A/V}^2$ ,  $\mu_p C_{ox}=65\mu\text{A/V}^2$ ,  $V_{tn}=-V_{tp}=0.6$  V,  $V_{An}(\frac{1}{\lambda_n})=20$  V,

$$|V_{Ap}|(\frac{1}{\lambda_p})=10\text{V}$$

(a). Draw the small-signal equivalent circuit. (3%)

(b). Calculate midband voltage gain  $A_M=v_o/v_i$ . (17)