

大同大學 101 學年度轉學入學考試試題

考試科目：電子學

系別：電機工程學系

第 1/1 頁

註：本次考試 不可以參考自己的書籍及筆記；不可以使用字典；可以使用計算器。

1. Given $R_1=5\text{ k}\Omega$, $R_2=10\text{ k}\Omega$, $V^+=5\text{ V}$, $V^-=-5\text{ V}$, diode cut-in voltage $V_{D0}=0.7\text{ V}$, diode resistance $r_D=0$, determine V_o , I_{D1} and I_{D2} for (a) $V_i=0\text{ V}$, (b) $V_i=4\text{ V}$. (12%) (Refer to Fig. P1.)
 (c). Draw the VTC (i.e. V_o vs V_i) plot, indicate the breakpoint point voltages and diode state (on or off) clearly.(13%)

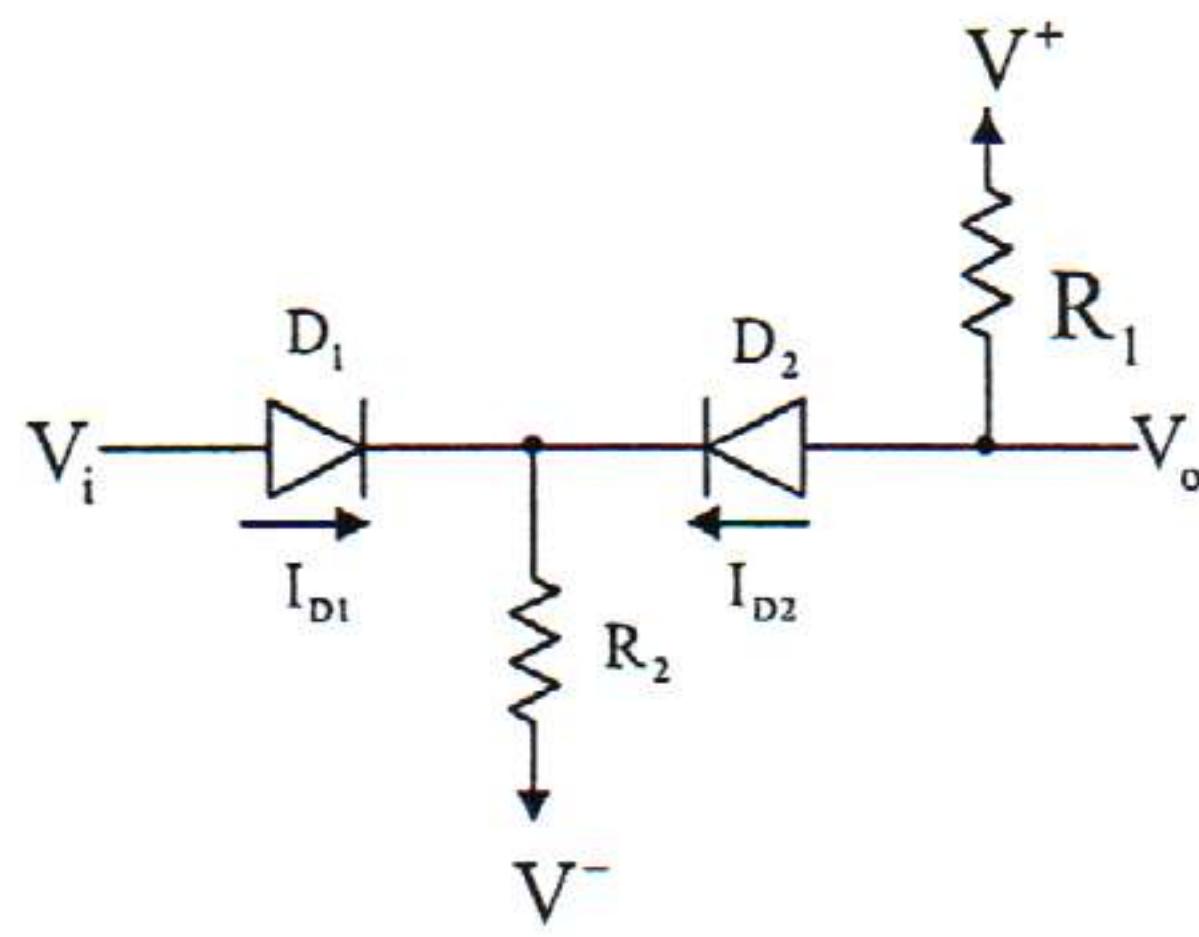


Fig. P1

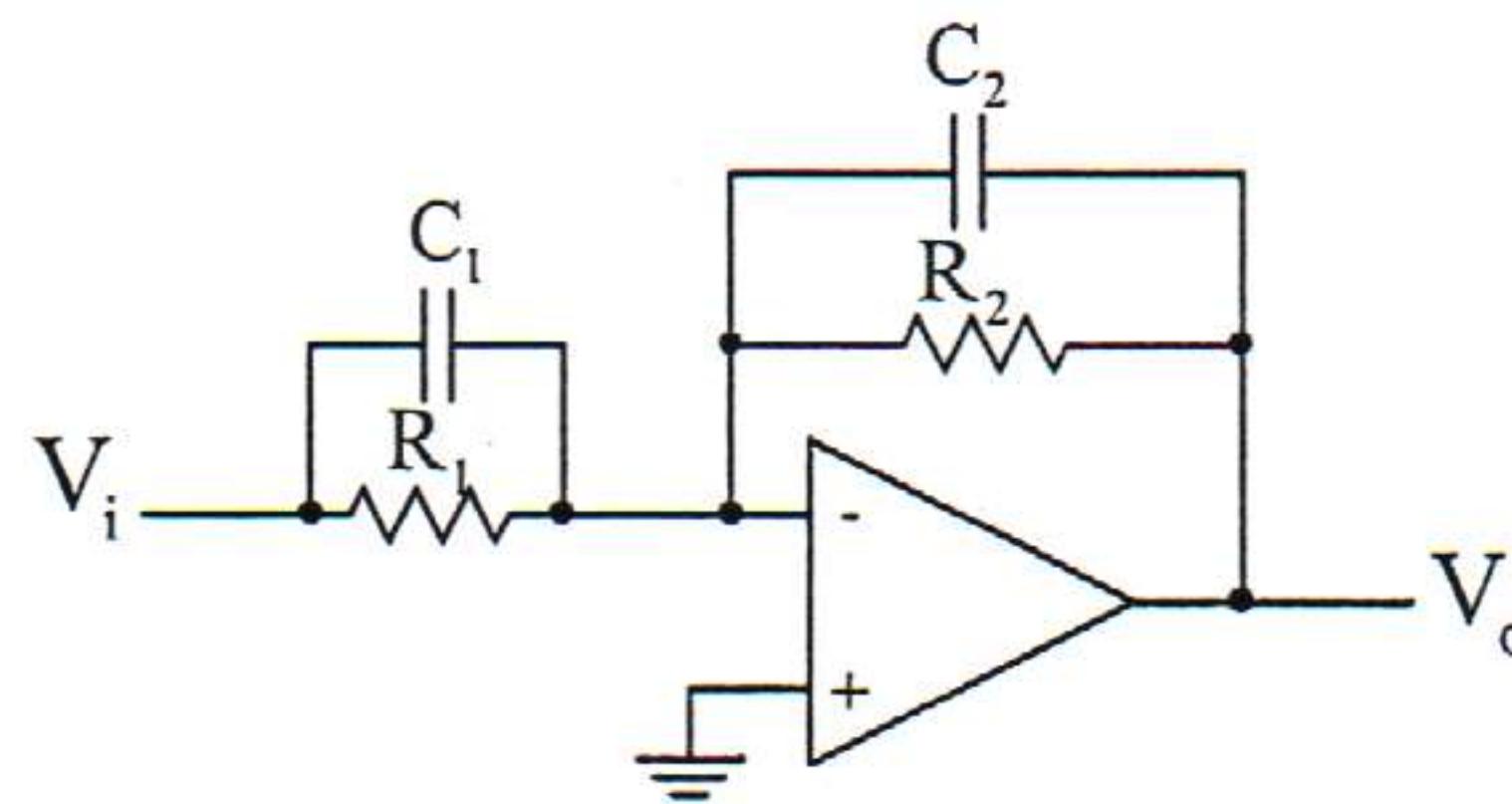


Fig. P2

2. (a). Derive the transfer function $T(s)=V_o/V_i$ of Fig. P2 (12%), in term of R , C , find the pole frequency ω_p , zero frequency ω_z , dc gain and high frequency gain. (8%)
 (b). If $R_2C_2 > R_1C_1$ draw the magnitude Bode plot $|T(j\omega)|=|T(s)|_{s=j\omega}$ vs ω qualitatively. (5%)
3. Refer to Fig. P3, BJT, $\beta=99$, bias current $I=1\text{ mA}$, $R_{sig}=5\text{ k}\Omega$, $R_B=100\text{ k}\Omega$, $R_C=10\text{ k}\Omega$, $R_E=0.225\text{ k}\Omega$ and $R_L=10\text{ k}\Omega$, neglect the BJT Early effect.
 (a). Draw the small-signal equivalent circuit (4%).
 (b). Calculate input resistance R_{in} (5%), midband voltage gain $G_v=\frac{V_o}{V_{sig}}$ (16%).

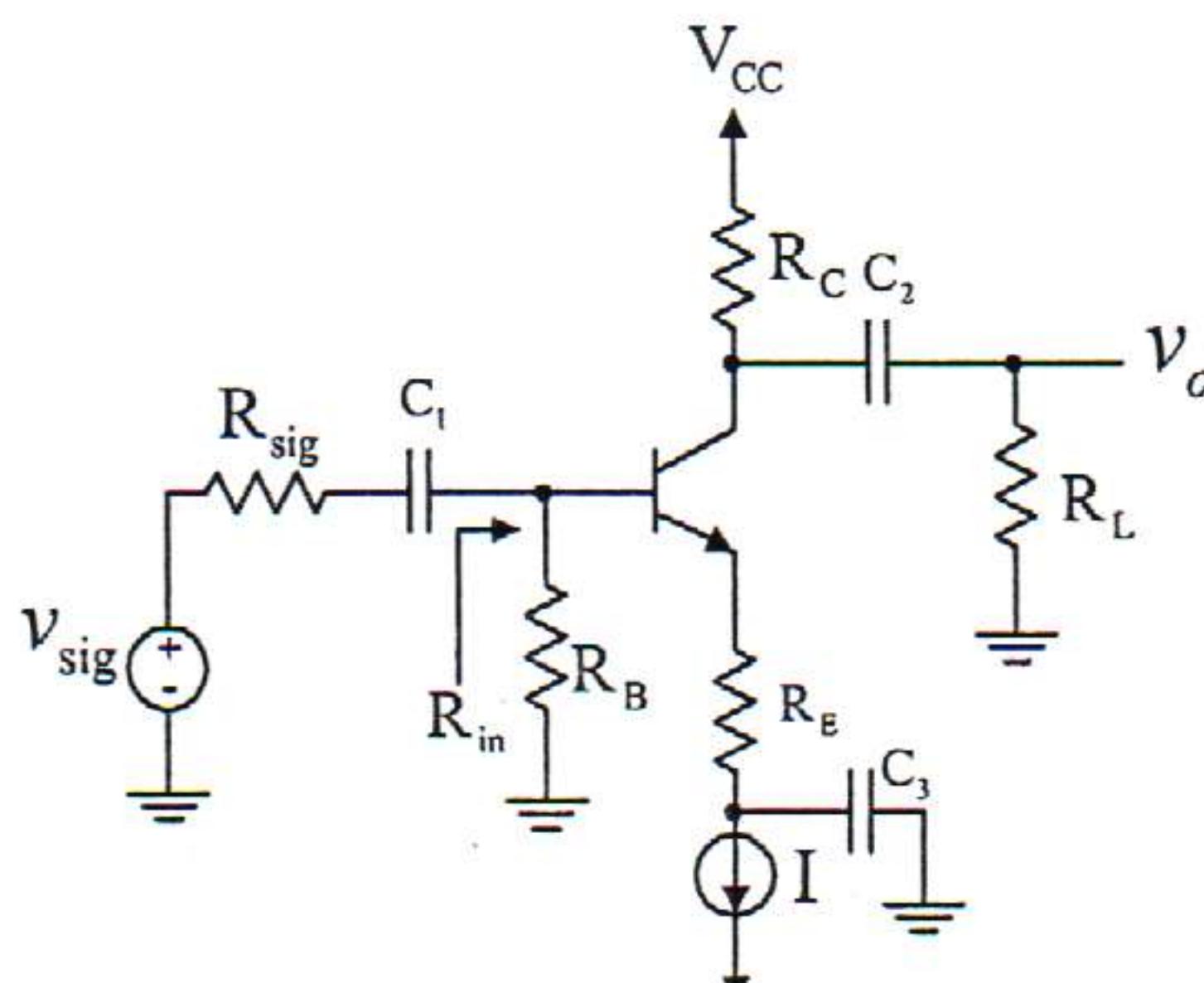


Fig. P3

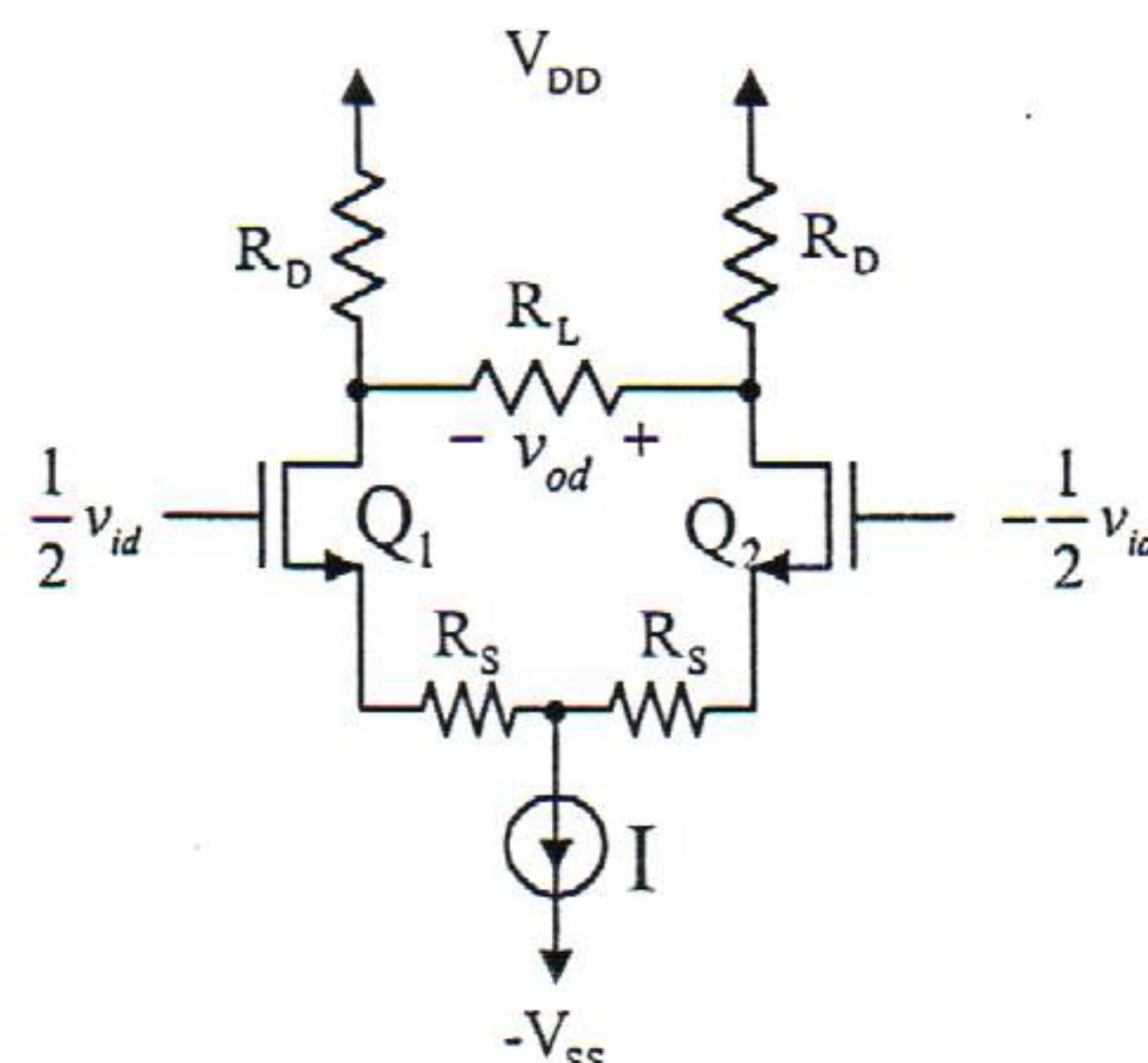


Fig. P4

4. (a). Neglect r_o , draw the differential half-circuit of Fig. P4, derive the differential voltage gain $A_d=\frac{V_{od}}{V_{id}}$.(10%)
 (b). Given biasing current $I=0.8\text{ mA}$, MOS W/L=100, $\mu_nC_{ox}=0.2\text{ mA/V}^2$, $R_D=10\text{ k}\Omega$, $R_L=20\text{ k}\Omega$
 $R_S=0.125\text{ k}\Omega$, calculate A_d .(15%)