

# 大同大學 106 學年度 (暑) 轉學入學考試試題

考試科目：電路學

系別：電機工程學系

第 1/2 頁

註：本次考試 不可以 參考自己的書籍及筆記；不可以 使用字典；可以 使用計算器。

一、簡答題：（每題10分，合計30分）

- 簡述下列定律：①克希荷夫電流定律（KCL）②希荷夫電電壓定律（KVL）③歐姆定律
- 何謂開路（open circuit）？何謂短路（short circuit）？何謂相依電源（dependent source）？
- 請分別寫出電容器與電感器之電壓-電流關係式及所儲存之能量各為何？

二、計算題：（每題10分，合計70分）

- Determine the minimum resistor size in the circuit of Fig. 1 that can be connected to a given battery without exceeding the resistor's  $1/4$  W power rating. **Known Quantities:** Battery voltages: 1.5 and 3 V.
- Determine the voltage  $v_3$  in the circuit of Fig. 2. **Known Quantities:**  $R_1 = 10 \Omega$ ;  $R_2 = 6 \Omega$ ;  $R_3 = 8 \Omega$ ;  $V_s = 3$  V.
- Determine the current  $i_1$  in the circuit of Fig. 3. **Known Quantities:**  $R_1 = 10 \Omega$ ;  $R_2 = 2 \Omega$ ;  $R_3 = 20 \Omega$ ;  $I_s = 4$  A.
- The Wheatstone bridge circuit is shown in Fig. 4. Please find the unknown resistance  $R_x$ .

**Known Quantities:**  $R_1 = R_2 = R_3 = 1 \text{ k}\Omega$ ,  $V_s = 12$  V, and  $V_{ab} = 12$  mV

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

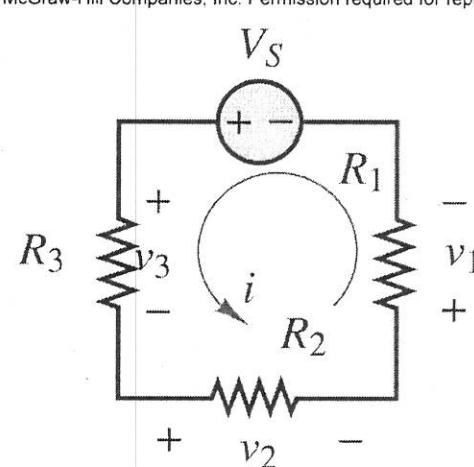
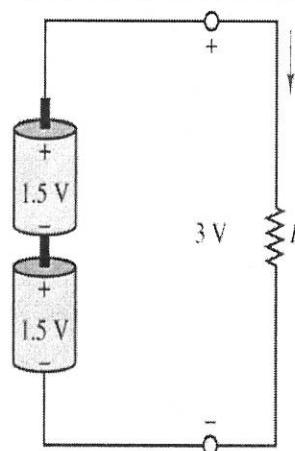
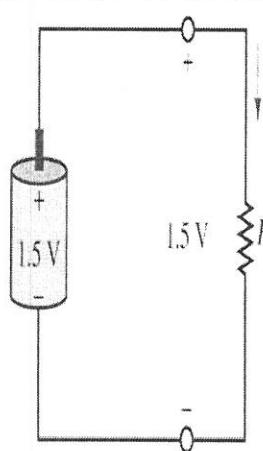


Fig. 1

Fig. 2

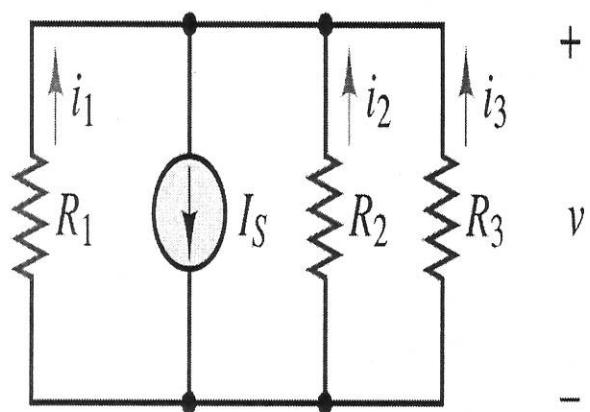


Fig. 3

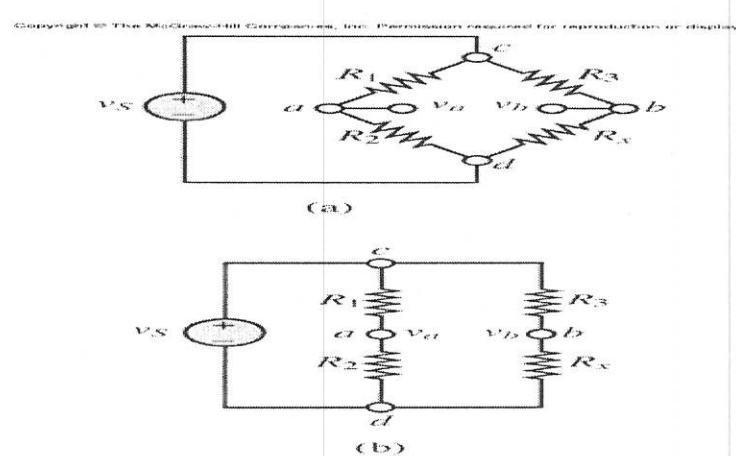


Fig. 4

背面繼續

5. Use node analysis to determine the current  $i$  flowing through the voltage source in the circuit of Fig. 5. Assume that  $R_1 = 2 \Omega$ ;  $R_2 = 2 \Omega$ ;  $R_3 = 4 \Omega$ ;  $R_4 = 3 \Omega$ ;  $I = 2 A$ ;  $V = 3 V$ .

6. Find the unknown voltage  $v_x$  in the circuit of Fig. 6.

**Given data:**  $V_s = 10 V$ ;  $I_s = 2 A$ ;  $R_1 = 5 \Omega$ ;  $R_2 = 2 \Omega$ ;  $R_3 = 4 \Omega$ .

7. Compute the Thevenin equivalent (open circuit voltage  $V_T$  and equivalent impedance  $Z_T$ ) of the circuit of Fig. 7.

**Known Quantities:**  $Z_1 = 5 \Omega$ ;  $Z_2 = j20 \Omega$ ;  $v_s(t) = 110\cos(377t) V$ .

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

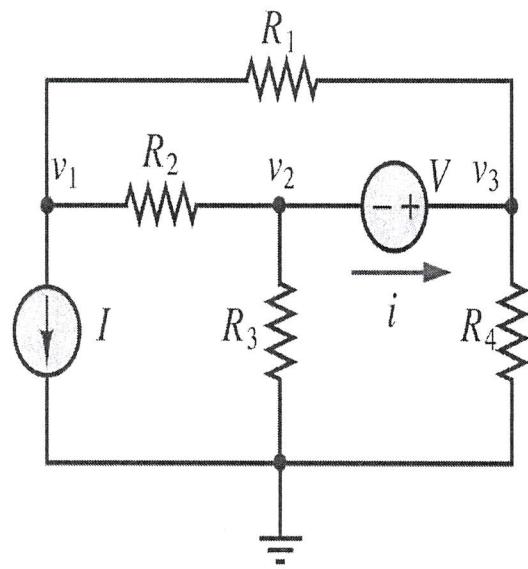


Fig. 5

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.


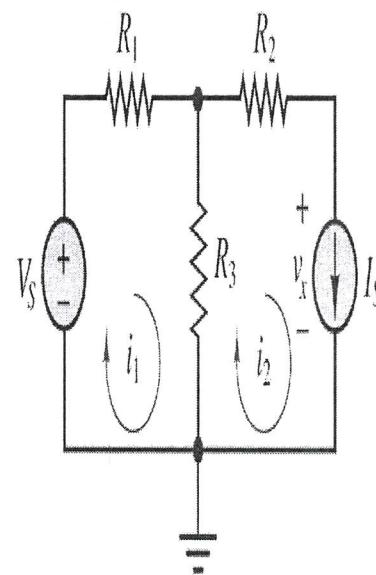


Fig. 6

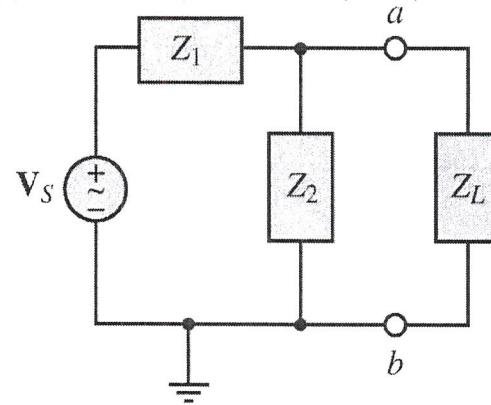Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



$$V_s = 110\angle 0^\circ V \quad Z_1 = 5 \Omega \quad Z_2 = j20 \Omega$$

Fig. 7