

大同大學 108 學年度 (暑)轉學入學考試試題

考試科目：電路學

系別：電機工程學系

第 1/1 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 不可以使用計算器。

1. In the circuit shown in Fig.1, determine v_x and the power absorbed by the $40\text{-}\Omega$ resistor. (20%)

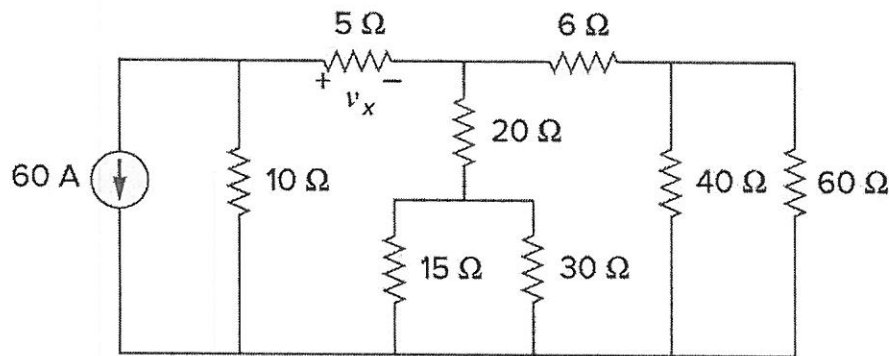


Fig.1

2. The circuit, which shown in Fig.2, is designed to control the output voltage by the environment light intensity. If the resistance of photo-resistor is $500\text{ k}\Omega$ and $1\text{ k}\Omega$ with or without light irradiation, respectively. (a) If the potentiometer (variation resistor, R_1) is set at $1\text{ k}\Omega$, calculate the output voltage (V_{out}). (b) If a yellow LED, whose turn on voltage (V_D) is around 2.0 V , is connected to the ourpur terminals, which resistance value of the potentiometer is fit to contral the LED on/off? (20%)

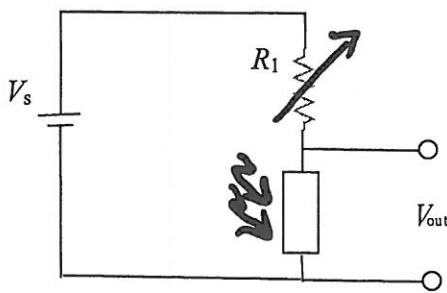


Fig.2

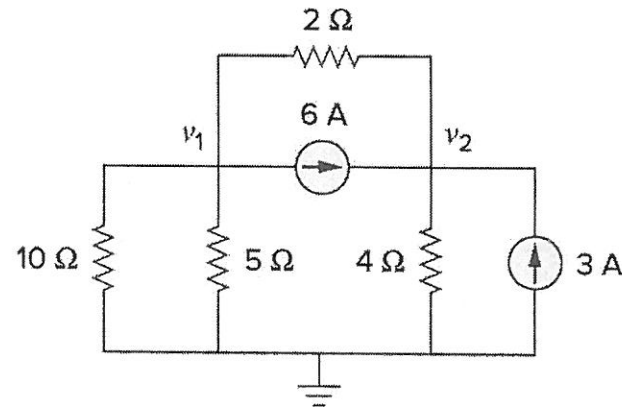


Fig.3

3. For the circuit in Fig.3, find the node voltage v_1 and v_2 . (20%)

4. (a) Define the meaning of the Thevenin equivalent in a circuit. (b) Find the Thevenin equivalent of the circuit in Fig.4 at the terminals a - b . Then find the current through $R_L=6\text{ }\Omega$. (20%)

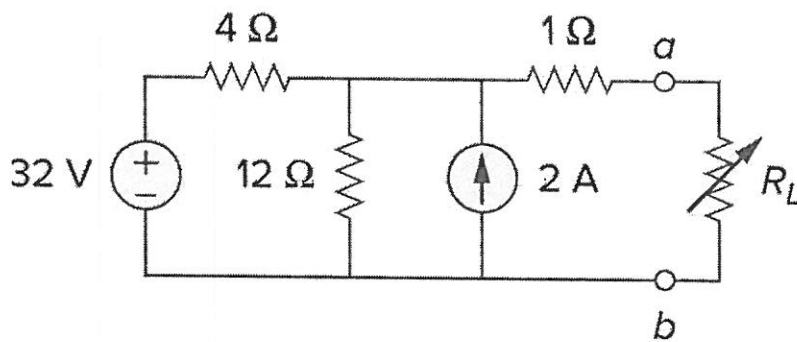


Fig.4

5. (a) What's the meaning of 1000 Ah ? (b) Calculate the charge stored on $3\text{-}\mu\text{F}$ capacitor with 20 V across it. (c) Find the energy Stored in the capacitor. (20%)