

大同大學 九十四 學年度 轉學考試 試題

科目名稱: 電路學

系別: 電機工程學系

第 1 頁, 共 1 頁

註: 本次考試 不可參考書籍及筆記

可使用計算器

不可參用字典

1. Apply mesh analysis to find i_1 , i_2 , and the power supplied by the current source of 2 A as shown in Fig. 1. (20%)

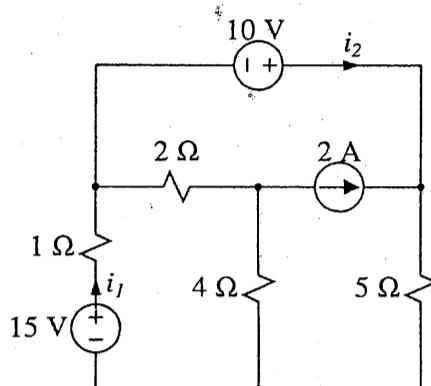


Fig. 1

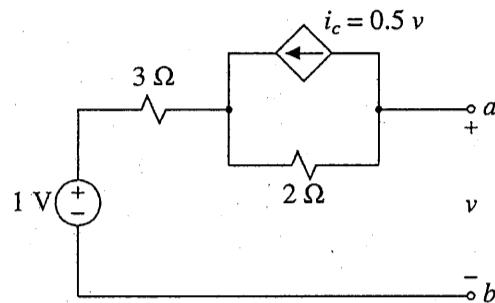


Fig. 2

2. Consider the circuit shown in Fig. 2.

- Find the Thévenin equivalent circuit. (15%)
- Find the value of a resistor connected across a , b to have the maximum power transferred and calculate the maximum power. (5%)

3. Consider the circuit shown in Fig. 3, where

$$i_s(t) = \begin{cases} -1 \text{ A} & t < 0 \\ 1 \text{ A} & t > 0 \end{cases}$$

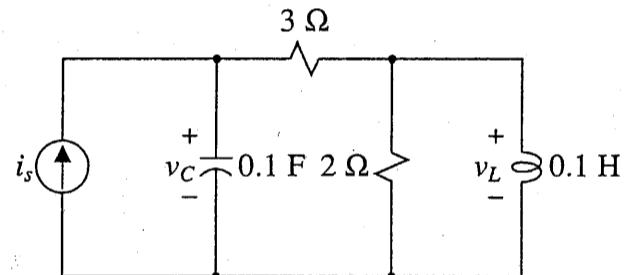


Fig. 3

4. The transformer circuit in Fig. 4 operates under steady-state condition. Find $i_1(t)$, $i_2(t)$, and $v_{out}(t)$ given that $v_s(t) = 5 \sin(1000t)$ V. (20%)

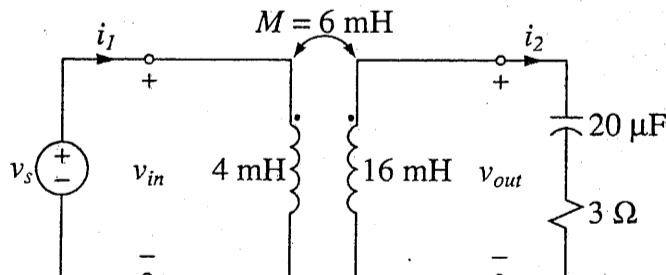


Fig. 4

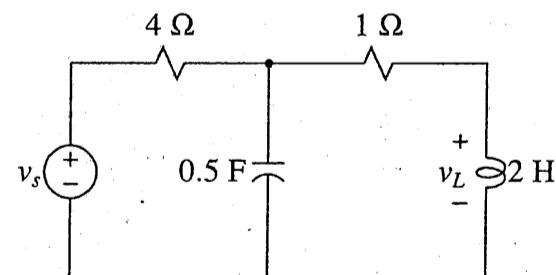


Fig. 5

5. For a circuit shown in Fig. 5,

- obtain the transfer function $H(s) = \frac{V_L}{V_s}$; (10%)
- find the forced response $v_L(t)$ when $v_s(t) = 2e^{-t} \cos(4t)$. (10%)