

大同大學 九十四 學年度 轉學考試 試題

考試科目：電子學

系別：電機工程學系 第 1 頁，共 1 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

1. Refer to Fig. P1, assuming the diodes to be ideal, derive the relationship between V_O and V_I . Sketch the transfer characteristic (i.e. V_O vs V_I plot) for $-10 \leq V_I \leq 10$, indicate the voltage at the breakpoints clearly and identify the state of diodes to be on or off in each region. (20%)

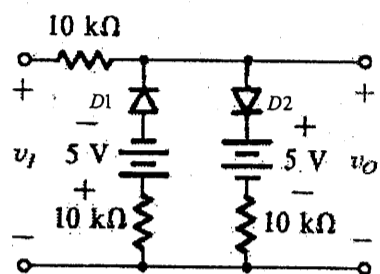


Fig. P1

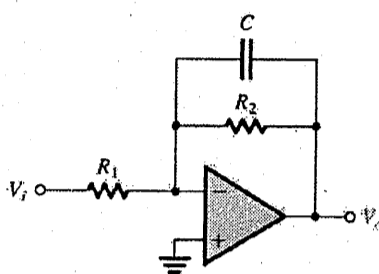


Fig. P2

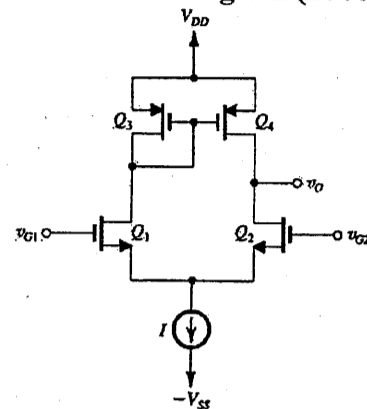


Fig. P3

2. (a). Refer to Fig. P2, assuming the OP. to be ideal, derive the transfer function $T(s) = \frac{V_O}{V_I}$ (8%)
 (b). Design the circuit to obtain the input resistance of $1\text{ K}\Omega$, a dc gain of 20dB, and a 3-dB frequency of 4 KHz. At what frequency does the magnitude of the transfer function reduce to unity? (16%)
3. Refer to Fig. P3, for n-MOS $(W/L)_n=100$, $\mu_n C_{ox} = 0.2\text{ mA/V}^2$, $\lambda_n = 0.05\text{ V}^{-1}$; for p-MOS, $(W/L)_p=200$, $\mu_p C_{ox} = 0.1\text{ mA/V}^2$, $\lambda_p = 0.05\text{ V}^{-1}$; current source, $I=0.8\text{ mA}$ with output resistance $R_{ss}=25\text{ K}\Omega$, $v_{G1} - v_{G2} = v_{id}$. Calculate transconductance (G_m), output resistance (R_o) of the differential amplifier and voltage gain (A_d) for the differential mode. (15%)

4. Fig. P4 shows the high-frequency equivalent circuit of a MOS amplifier, use the parameters shown in the circuit.

- (a). Derive an expression for the low frequency voltage gain $\frac{V_O}{V_{sig}}$. (6%)

- (b). Using OCTC (open-circuit time constants) method to derive the time constants τ_{gs} for C_{gs} , τ_{gd} for C_{gd} and write an expression for the upper 3dB frequency f_H for the circuit. (15%)

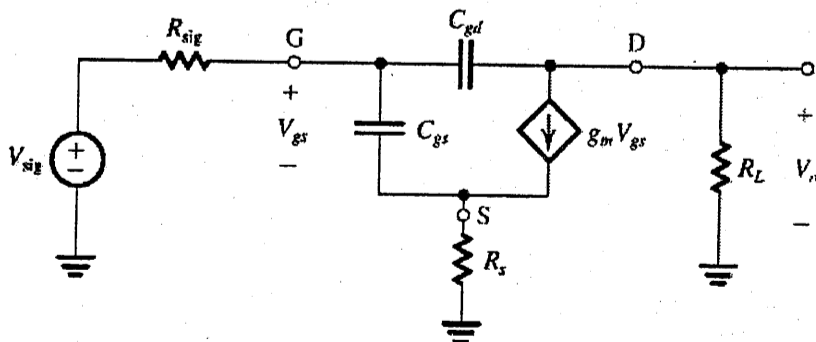


Fig. P4

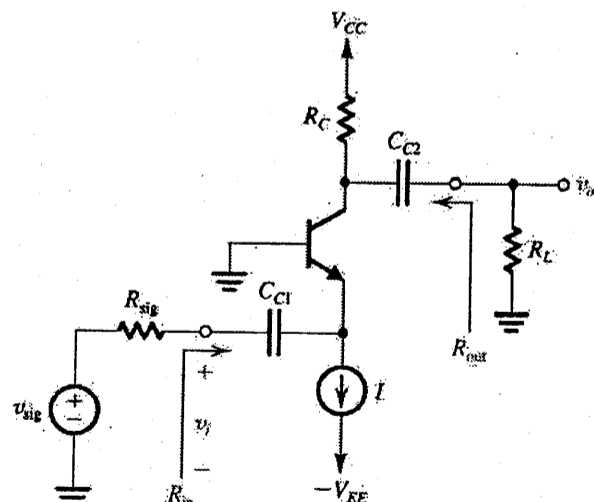


Fig. P5

5. Refer to Fig. P5, neglect BJT's r_o , $I=1\text{ mA}$, $\beta=100$, $R_{sig}=R_L=5\text{ K}\Omega$, and $R_C=8\text{ K}\Omega$.

Calculate R_{in} , R_{out} , $A_v = \frac{v_o}{v_i}$, and $G_v = \frac{v_o}{v_{sig}}$. (20%)