

# 大同大學 97 學年度轉學入學考試試題

考試科目：電路學

所別：電機工程學系

第 2/2 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

<接前頁>

- (4) Refer to the circuit shown in Fig. 4.
- (a) What is the power factor? (6%)
  - (b) What is the average power dissipated? (6%)
  - (c) What is the value of the capacitance that will give a unity power factor when connected to the load? (8%)



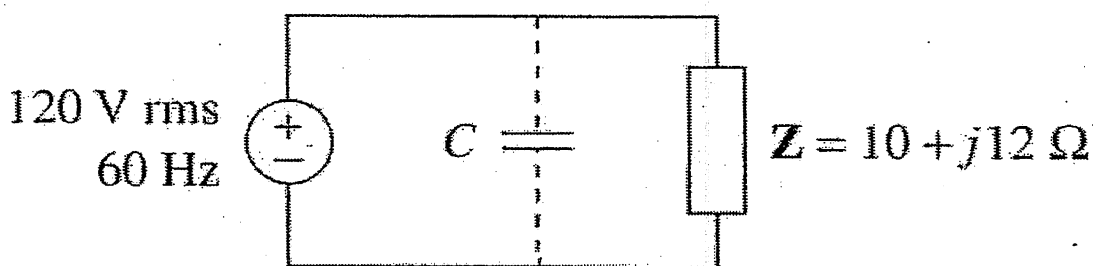


Fig. 4

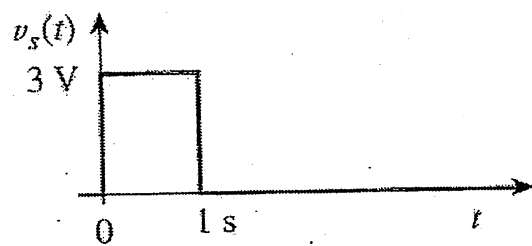- (5) (a) Find the Laplace transform of the voltage shown in Fig. 5(a). (8%)
- (b) Using that value of  $v_s(t)$  in the circuit shown in Fig. 5(b), find the value of  $v_o(t)$ . (12%)



(a)

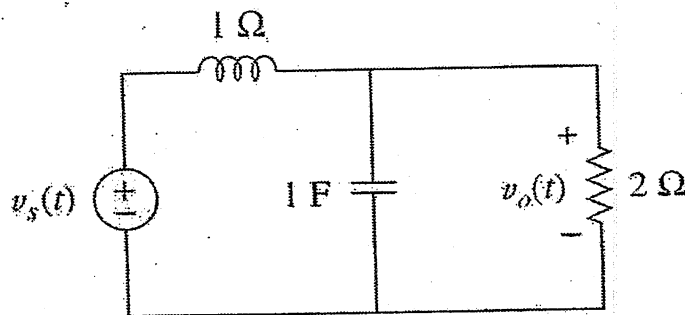

(b)

Fig. 5

# 大同大學 97 學年度轉學入學考試試題

考試科目：電路學

所別：電機工程學系

第 1/2 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

- (1) Three capacitors,  $C_1 = 5\mu F$ ,  $C_2 = 10\mu F$ , and  $C_3 = 20\mu F$ , are connected in parallel across a 150-V source. Determine :
- the total capacitance, (6%)
  - the charge on each capacitor, (6%)
  - the total energy stored in the parallel combination. (8%)

- (2) Use nodal analysis to find  $V_o$  in the circuit of Fig. 2. (20%)

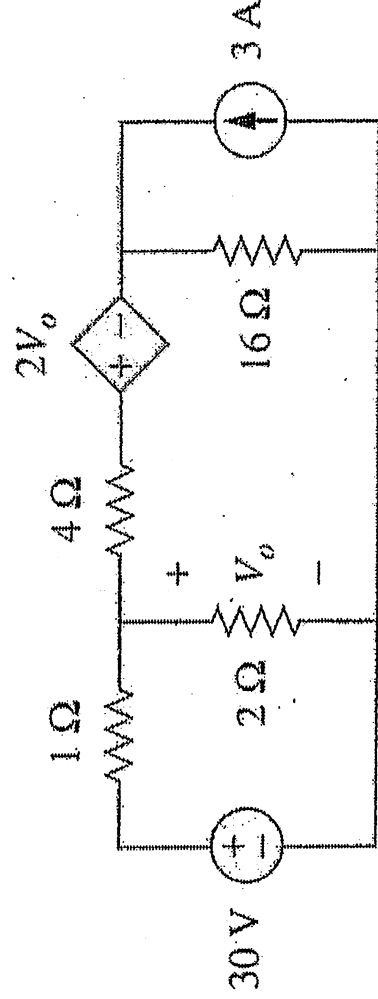


Fig. 2

- (3) By using mesh analysis, find  $I_1$  and  $I_2$  in the circuit depicted in Fig. 3. (20%)

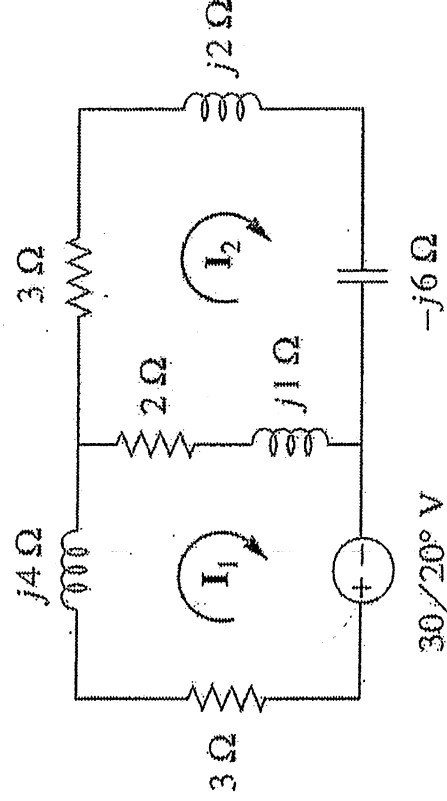


Fig. 3