

# 大同大學 98 學年度轉學入學考試試題

考試科目：電子學

所別：電機工程學系

第 1/1 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

1. Refer to Fig. P1, diode cut-in voltage  $V_{D0}=0.7\text{ V}$ ,  $r_D=0$

(a). Draw VTC ( $v_o$  vs  $v_i$ ) plot. (10%)

(b). Draw the output waveform,  $v_o$  vs  $t$  plot for  $0 \leq \omega t \leq 4\pi$ . Indicate the breakpoints clearly. (10%)

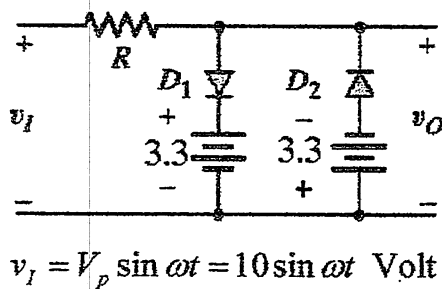


Fig. P1

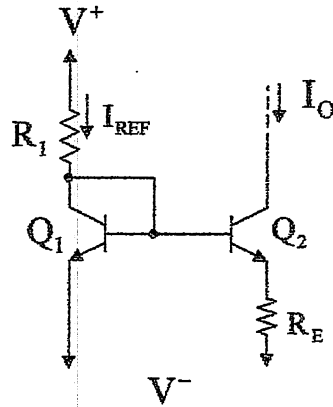


Fig. P2

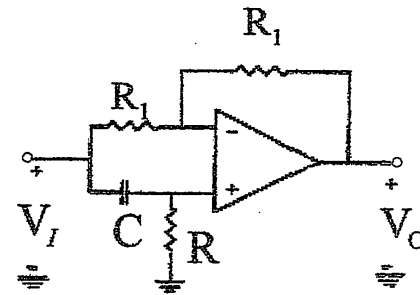


Fig. P3

2. (a). Refer to Fig. P2, state the assumption, derive the relationship between  $I_o$  and  $I_{REF}$ . (10%)

(b).  $V^+=5\text{V}$ ,  $V^-=-5\text{V}$ ,  $I_{REF}=1\text{ mA}$ , to generate a constant current  $I_o=12\text{ }\mu\text{A}$ , determine the value of  $R_1$ ,  $R_E$ , assuming that  $V_{BE}=0.7\text{ V}$  at  $I_C=1\text{ mA}$ . (10%)

3. (a). Refer to Fig. P3, for the ideal op amp derive the transfer function  $T(s) = \frac{V_o}{V_i}$ . (10%)

(b). Derive an expression for the magnitude  $|T(j\omega)|$  and phase  $\phi(\omega)$ ,

$T(s)|_{s=j\omega} = T(j\omega) = |T(j\omega)|e^{j\phi}$ , plot  $|T(j\omega)|$  vs  $\omega$ ,  $\phi$  vs  $\omega$  (10%)

4.  $I_{REF}=100\text{ }\mu\text{A}$ ,  $\mu_n C_{ox}=90\text{ }\mu\text{A/V}^2$ ,  $\mu_p C_{ox}=30\text{ }\mu\text{A/V}^2$ ,  $V_{tn}=-V_{tp}=0.5\text{ V}$ ,  $1/\lambda_n=12.8\text{ V}$ ,  $1/|\lambda_p|=19.2\text{ V}$ .

$V_{DD}=V_{SS}=5\text{ V}$ , Assume MOS  $W/L=100\text{ }\mu\text{m}/1.6\text{ }\mu\text{m}$  for all MOSs. (Neglect channel length modulation in DC calculation) (Refer to Fig. P4)

(a) Calculate  $R_{REF}$ . (6%)

(b) Calculate voltage gain  $v_o/v_i$ . (14%)

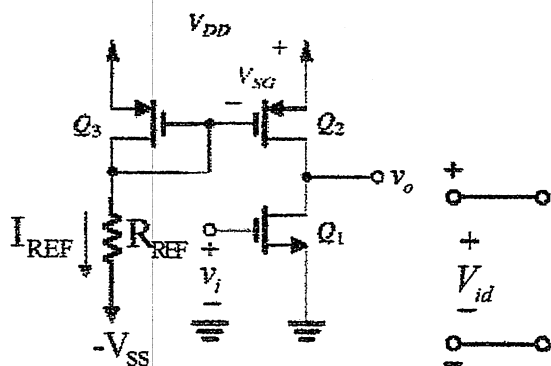


Fig. P4

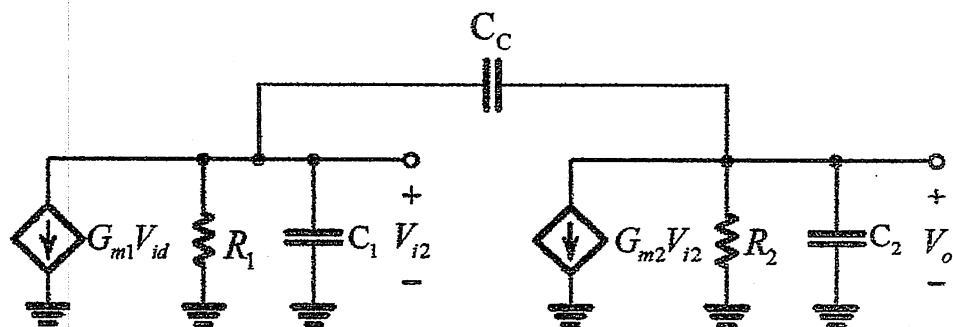


Fig. P5

5. Refer to Fig. P 5, the equivalent circuit of 2-stage amplifier.

Neglect capacitances  $C_1$  and  $C_2$  and use Miller approximation, the voltage gain can be written as  $A(s) = \frac{V_o}{V_{id}} = \frac{A_0}{1 + \frac{s}{\omega_p}}$

Given  $G_{m1}=60\text{ }\mu\text{A/V}$  and  $G_{m2}=100\text{ }\mu\text{A/V}$ ,  $R_1=1\text{ M}\Omega$ ,  $R_2=2\text{ M}\Omega$ ,  $C_c=10\text{ PF}$ .

(a). Calculate the dc voltage gain  $A_0 = \frac{V_o}{V_{id}}$  (10%).

(b). Neglect capacitances  $C_1$  and  $C_2$ , write an expression for the dominant pole frequency ( $\omega_p$ ) due to  $C_c$  in terms of  $R_i$ ,  $C_i$  and  $G_{mi}$  ( $i=1, 2$ ). Calculate  $\omega_p$  and unity gain frequency  $\omega_{t,1}$ . (10%)